

Circuit Connections

1. IR Sensor:

- Connect the **output pin** of the **IR sensor** to **digital pin 5** on the **Arduino**.
- Connect the **power pin** of the IR sensor to the **power supply (5V)**.
- Connect the **ground pin** of the IR sensor to **GND**.

2. Servo Motor:

- Connect the **ground pin** of the **servo motor** to the **ground rail (GND)**.
- Connect the **power pin** of the servo motor to the **power supply (5V)**.
- Connect the **control pin** of the servo motor to **digital pin 3** on the **Arduino**.

Working

- When **button 1** is pressed, the **servo motor** rotates to **45 degrees**, then returns to its initial position after **1000ms** (1 second).
- When **button 2** is pressed, the **servo motor** rotates to **90 degrees**, then returns to its initial position after **1000ms**.

- When **button 3** is pressed, the **servo motor** rotates to **135 degrees**, then returns to its initial position after **1000ms**.
- When **button 4** is pressed, the **servo motor** rotates to **180 degrees**, then returns to its initial position after **1000ms**.