Circuit Connections:

• ATtiny85:

- Connect its power pin to the battery's positive terminal.
- Connect its ground pin to the battery's negative terminal.

• TMP36 Temperature Sensor:

- o Connect the power pin to the battery's positive terminal.
- Connect the ground pin to the battery's negative terminal.
- Connect the Vout pin to PB2 of the ATtiny85.

LED and Resistor:

- Connect the anode of the LED to PB0 of the ATtiny85.
- Attach one end of a resistor to the LED's cathode.
- Connect the other end of the resistor to the ATtiny85's ground.

Working Principle:

After assembling the components as per the circuit diagram, the temperature sensor's output determines the LED's blinking pattern based on predefined temperature thresholds set in the code.