

A **Capacitance Meter** measures the value of a capacitor in **farads** using an **Arduino**. Here's a brief overview of how to build it in Tinkercad:

Components Needed:

- **Arduino Uno**
- **LCD display (16x2)**
- **Capacitor** (the one you want to measure)
- **Resistor** (typically 1kΩ)
- **Pushbutton** (optional, for triggering measurement)
- **Breadboard and jumper wires**

Circuit Setup:

1. Arduino Pin Connections:

- Connect a **resistor** and the **capacitor** in series between a digital pin (e.g., **D2**) and **ground (GND)**.
- Use a **digital pin** (e.g., **D3**) to measure the capacitor's charging time using Arduino's **pulseIn()** function.
- Connect the **LCD display** (pins for **VCC**, **GND**, **SDA**, **SCL**) to the Arduino to show the measured capacitance.

2. Code:

- Write the code to measure the **charging time** of the capacitor.

where **t** is the charging time and **R** is the known resistor value.

3. Display Output:

- The Arduino will display the capacitance value on the **LCD** screen in **farads**.